

CS2323 Computer Architecture

Mid-Term Submission - RISC-V Processor Implementation

Abhimanyu Koushik Garimella
EE24BTECH11024

October 2025

Introduction

This document details the progress on the RV64IMD processor implementation project. The focus has been on designing and implementing the core datapath components. These fundamental building blocks form the foundation of the non-pipelined baseline processor that will eventually be extended to support the full RV64IMD instruction set with pipelining. The complete datapath designed for a single-cycle processor is presented below.

Arithmetic and Logic Unit

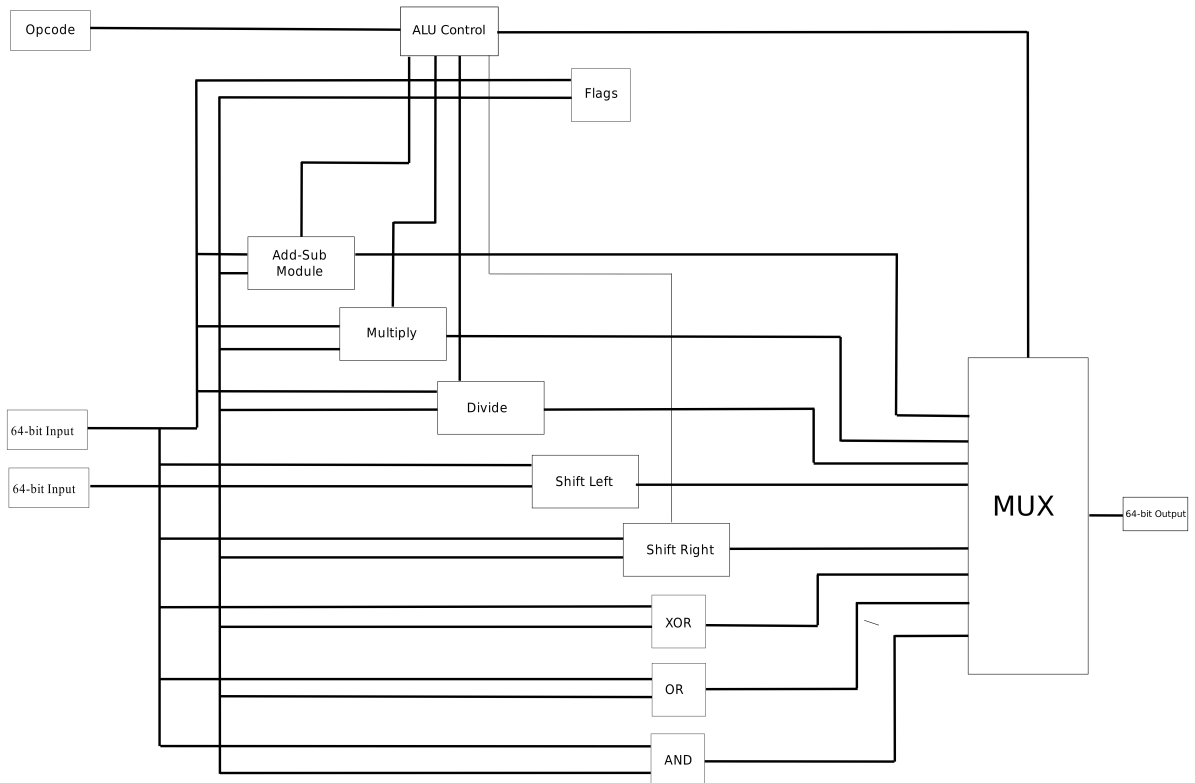


Figure 1: ALU Block

The task of the ALU is to take the input values from the input ports, perform the specific operation specified by the ALUOp, and send back the output. All operations specified in the RISC-V instruction set are implemented. Each operation was performed directly in Verilog using the provided operations, with careful consideration given to understanding how each operation is implemented. The output for all operations is calculated simultaneously, and a final multiplexer is used to select the correct output, with the select lines for the multiplexer being the ALUOp codes.

Addition-Subtraction Block

The task of the Addition-Subtraction block is to perform addition, subtraction, set less than, and set less than unsigned operations. For addition and subtraction, a basic 64-bit addition block is used. One of the inputs is taken directly from the inputs of the ALU, while the other input is selected by a multiplexer whose inputs are the second input and its negative. The select line for the multiplexer comes from the ALU Control.

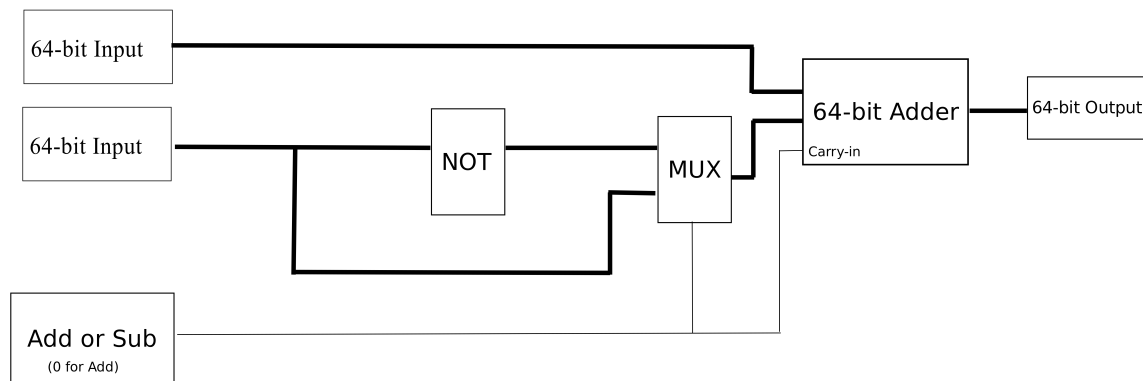


Figure 2: Addition-Subtraction Block

Shift Operations

Shift operations are essential for bit manipulation and multiplication/division by powers of 2. The RISC-V ISA specifies three types of shifts: logical left, logical right, and arithmetic right.

The shift left operation performs logical left shifts by inserting zeros from the right. For a 64-bit operand, the shift amount ranges from 0 to 63 bits. It was designed as shown below.

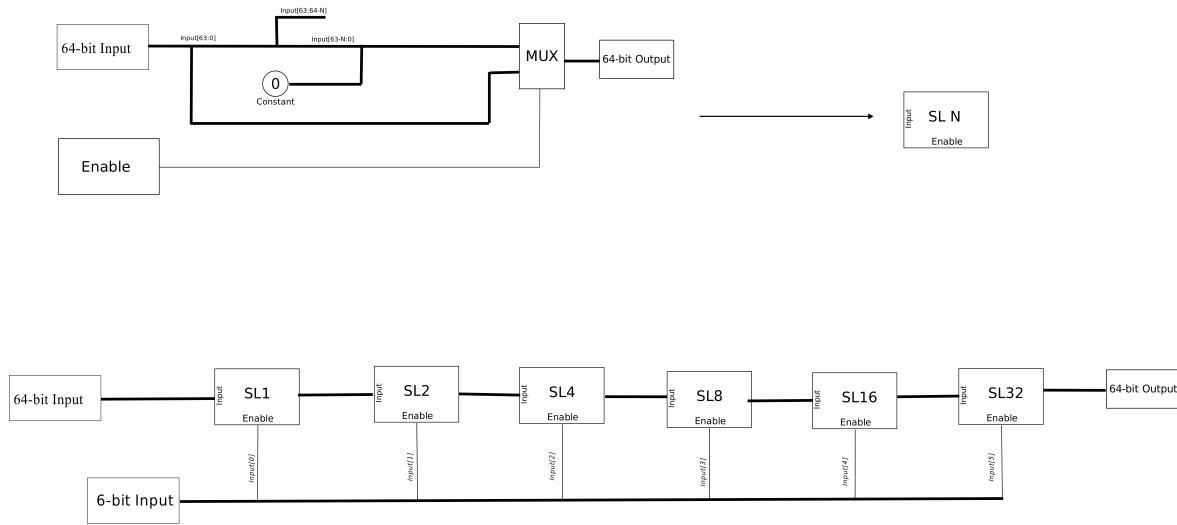


Figure 3: Shift Left Block

The shift right operation performs logical right shifts by inserting zeros or ones from the left. For a 64-bit operand, the shift amount ranges from 0 to 63 bits. It was designed as shown below.

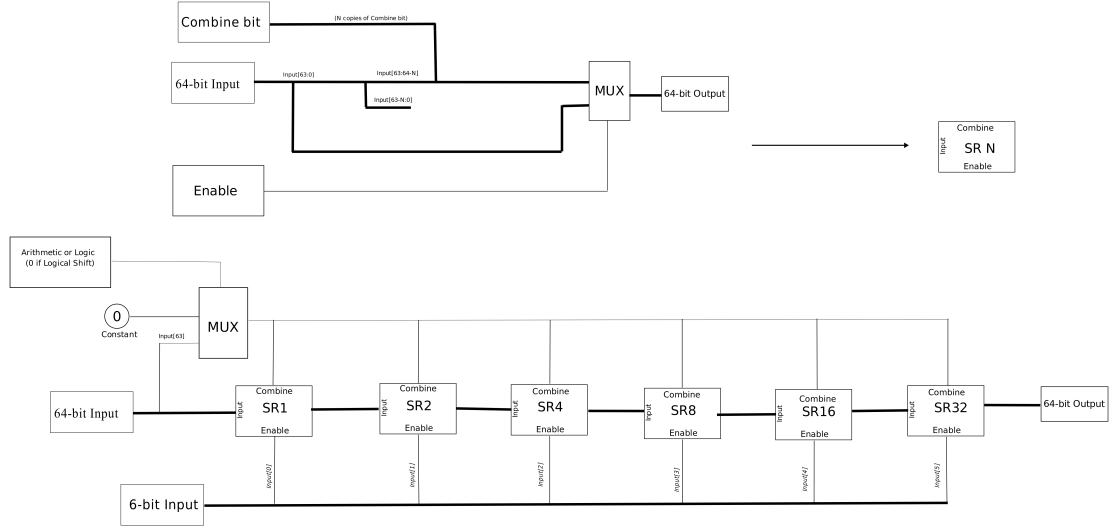


Figure 4: Shift Right Block

A control signal selects between logical and arithmetic mode. For arithmetic shifts, the most significant bit is used as the fill value.

Unsigned Multiplier

The M-extension of RISC-V requires hardware multiplication support. The multiplier unit implements unsigned multiplication for 64-bit operands.

The multiplier uses an iterative add-and-shift algorithm. For two n -bit numbers A and B , the product is computed as:

$$P = \sum_{i=0}^{n-1} A \cdot B_i \cdot 2^i$$

where B_i is the i -th bit of B .

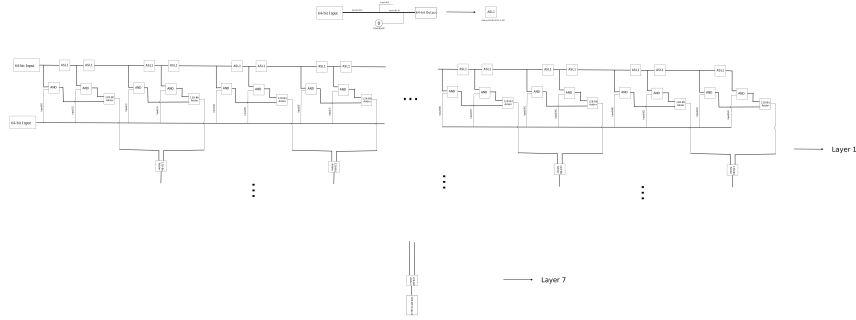


Figure 5: Unsigned Multiplier Architecture

Once all the partial sums are calculated, they are added in parallel manner.

For signed multiplication (MULH, MULHSU), the operands are converted to unsigned values, multiplied, and the result is adjusted based on the original signs.

Unsigned Divider

Division is more complex than multiplication and requires careful handling of edge cases. The divider implements unsigned division and produces both quotient and remainder.

The divider uses a restoring division algorithm. For dividend N and divisor D , it computes quotient Q and remainder R such that:

$$N = Q \cdot D + R, \quad 0 \leq R < D$$

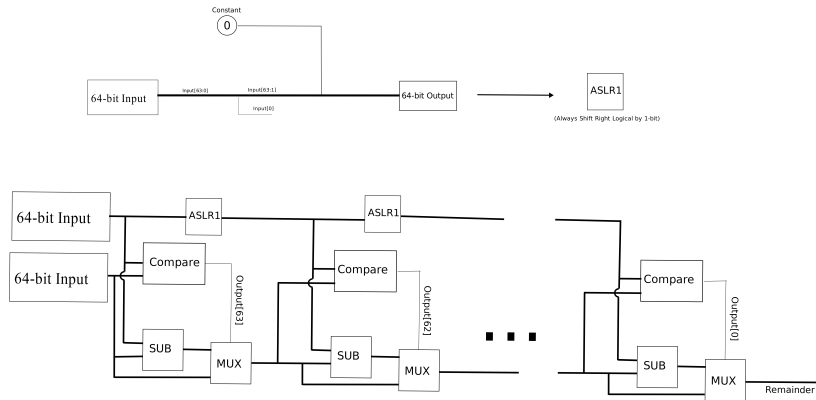


Figure 6: Unsigned Divider Architecture

The algorithm works by repeatedly subtracting the divisor from the dividend. If the subtraction produces a non-negative result, a 1 is placed in the quotient and the remainder is updated. Otherwise, a 0 is placed in the quotient and the remainder is restored.

Explaining the Datapath

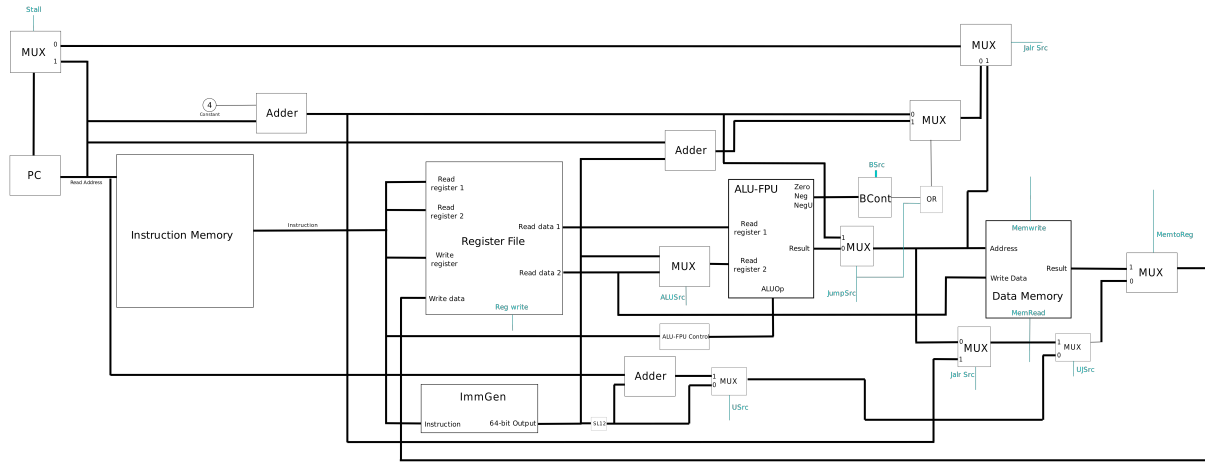


Figure 7: Complete Single-Cycle Processor Datapath

R-format Instruction Path

- R-format instructions execute through a well-defined datapath sequence. The instruction is first retrieved from the Instruction Memory, where the bits corresponding to the source and destination registers are extracted and forwarded to the Register File. The Register File outputs the values stored in the specified source registers.
- The Control Unit (not shown in the diagram) configures the ALUSrc control signal such that the multiplexer selects the source register value rather than an immediate. These operands are then routed to the ALU-FPU block, where the ALU-FPU control signals determine the specific arithmetic or logical operation to be performed. The ALU-FPU output is connected to the address port of the Data Memory; however, the MemRead and MemWrite control signals remain deasserted to prevent unintended memory modifications.
- The ALU-FPU result is also directed to a multiplexer that selects between the ALU-FPU output and data retrieved from memory. For R-format instructions, the multiplexer select signal is configured to choose the ALU-FPU output, which is then written to the destination register by asserting the RegWrite control signal in the Register File.

I-format Instruction Path

- Similar to R-format instructions, the I-format instruction is first retrieved from the Instruction Memory, where the bits corresponding to the source and destination registers are extracted and forwarded to the Register File. The Register File outputs the values stored in the specified source registers.
- The Control Unit configures the **ALUSrc** control signal such that the multiplexer selects the immediate value rather than the source register value. These operands are then routed to the ALU-FPU block, where the ALU-FPU control signals determine the specific arithmetic or logical operation to be performed. The ALU-FPU output is connected to the address port of the Data Memory. For load operations, the **MemRead** control signal is asserted while the **MemWrite** control signal remains deasserted to prevent unintended memory modifications.
- The ALU-FPU result is directed to a multiplexer that selects between the ALU-FPU output and data retrieved from memory. For load instructions, the multiplexer select signal is configured to choose the memory output, which is then written to the destination register by asserting the **RegWrite** control signal in the Register File. For non-load I-format instructions, the datapath flow follows the same sequence as R-format instructions.
- For the **jalr** instruction, the value **PC+4** is forwarded to two multiplexers (controlled by **JumpSrc** and **UJSrc** select lines), which configure the destination register to receive **PC+4**. To compute $PC = rs1 + imm$, the ALU is utilized. A multiplexer selects between this computed value and **PC+4** for the next program counter value, with the selection controlled by the **JalrSrc** signal.

B-format Instruction Path

For B-format instructions, the condition flags from the ALU are utilized instead of the ALU result itself. These flags determine whether **PC+imm** or **PC+4** becomes the next program counter value. The branch conditions are evaluated in the Branch Control block (**BCont**), with the specific branch condition type specified by the **BSrc** signal from the Control Unit. When the branch condition evaluates to true, the branch control signal is asserted and **PC+imm** is selected; otherwise, **PC+4** is selected to continue sequential execution.

J-format Instruction Path

The execution process for J-format instructions is nearly identical to the **jalr** instruction, except that instead of using the ALU to compute $rs1 + imm$, a dedicated adder with inputs **PC** and **imm** is employed to calculate the target address.

S-format Instruction Path

For S-format instructions, the effective address $rs1 + imm$ is calculated through the ALU block, similar to I-format instructions. The value from register **rs2** is connected to the Write Data port of the Data Memory, and the **MemWrite** control signal is asserted to write the data to memory at the computed address.

U-format Instruction Path

A dedicated adder is placed adjacent to the immediate generation block. After the generated immediate is shifted left by 12 bits, a multiplexer controlled by the **USrc** signal selects between the two U-format operations: **lui** (load upper immediate) loads the shifted immediate directly, while **auipc** (add upper immediate to PC) adds the shifted immediate to the current program counter value.

Conclusion

The fundamental arithmetic and logic components of the RV64IM processor have been successfully designed and implemented. These units form the execution core that will be integrated into the complete datapath.

The modular design approach allows for thorough testing at each level and will facilitate the transition to a pipelined architecture in Phase 2 of the project.